

# Recitation Class 9 (Examples)


Teaching Assistant  
Xie Jinglei



---

# RLC circuits

# RLC circuits

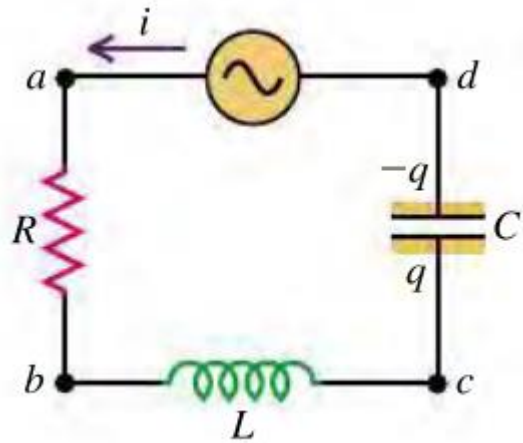

In the series circuit of Fig. 31.13a, suppose  $R = 300 \, \Omega$ ,  $L = 60 \, \text{mH}$ ,  $C = 0.50 \, \mu\text{F}$ ,  $V = 50 \, \text{V}$ , and  $\omega = 10,000 \, \text{rad/s}$ . Find the reactances  $X_L$  and  $X_C$ , the impedance  $Z$ , the current amplitude  $I$ , the phase angle  $\phi$ , and the voltage amplitude across each circuit element.

Find amplitude only

# RLC circuits

**31.61** • A resistance  $R$ , capacitance  $C$ , and inductance  $L$  are connected in series to a voltage source with amplitude  $V$  and variable angular frequency  $\omega$ . If  $\omega = \omega_0$ , the resonance angular frequency, find (a) the maximum current in the resistor; (b) the maximum voltage across the capacitor; (c) the maximum voltage across the inductor; (d) the maximum energy stored in the capacitor; (e) the maximum energy stored in the inductor. Give your answers in terms of  $R$ ,  $C$ ,  $L$ , and  $V$ .



---

**Waves**

# Waves

Recall (summer semester): classical wave equation (in 1D)


$$\frac{\partial^2 \xi}{\partial x^2} = \frac{1}{v^2} \frac{\partial^2 \xi}{\partial t^2}$$

displacement

phase speed



# Waves

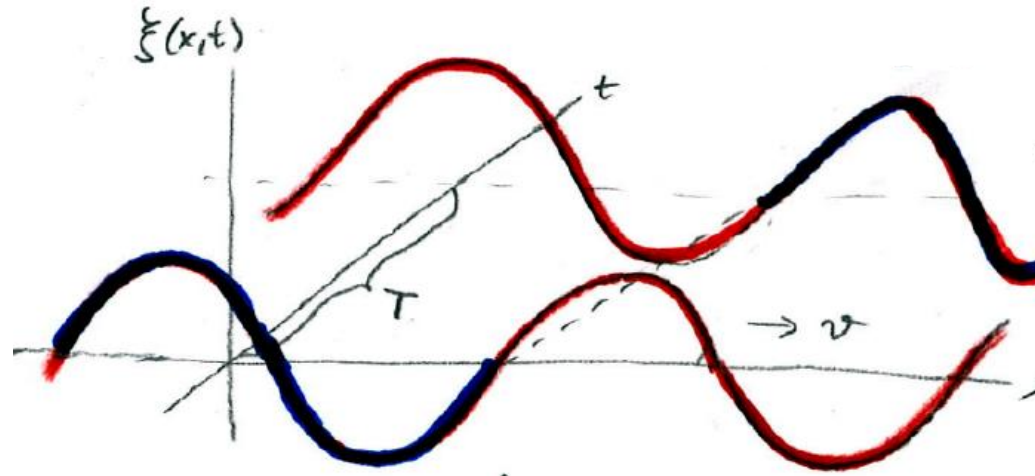

$$\xi(x,t) = A \cos(kx - \omega t + \varphi) \quad \rightarrow \text{right-travelling}$$

$$\xi_{\leftarrow}(x,t) = A \cos(kx + \omega t - \varphi) = \quad \leftarrow \text{left-travelling}$$

$$= A \cos[-(-kx - \omega t + \varphi)] \stackrel{\text{even}}{=} A \cos(-kx - \omega t + \varphi)$$

Note.  $\xi \leftrightarrow \xi_{\leftarrow}$   $k \leftrightarrow -k$