


## PROBLEM SET 9

Due: 22 November 2019, 12.30 p.m.

**Problem 1.** Consider two light bulbs connected in series around a solenoid (see figure (A)) producing a sinusoidally varying magnetic field. If we alter the circuit by connecting a thick copper wire across the circuit (see figure (B)), we find that the top bulb gets much brighter and the bottom one no longer glows.

*Why does this happen?*

(2 points)

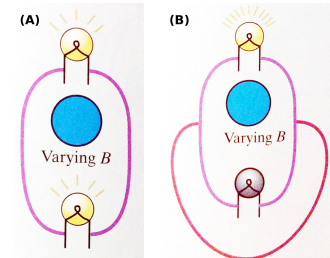

**Problem 2.** (*coaxial cable*) A small solid conductor with radius  $a$  is supported by insulating, non-magnetic disks on the axis of a thin-walled tube with inner radius  $b$ . The inner and outer conductors carry equal currents  $i$  in opposite directions. (a) Use Amperes law to find the magnetic field at any point in the volume between the conductors. (b) Write the expression for the flux  $d\Phi_B$  through a narrow strip of length  $l$  parallel to the axis, of width  $dr$ , at a distance  $r$  from the axis of the cable and lying in a plane containing the axis. (c) Integrate your expression from part (b) over the volume between the two conductors to find the total flux produced by a current  $i$  in the central conductor. (d) Show that the inductance of a length  $l$  of the cable is

$$L = l \frac{\mu_0}{2\pi} \ln \left( \frac{b}{a} \right).$$


(e) What is the energy stored in the magnetic field for a length  $l$  of this cable?

(3/2 + 3/2 + 1 + 1/2 + 1/2 points)

**Problem 3.** Two coils are wrapped around a cylindrical form in such a way that the same flux passes through every turn of both coils. (In practice this is achieved by inserting an iron core through the cylinder; this has the effect of concentrating the flux.) The "primary" coil has  $N_1$  turns and the "secondary" has  $N_2$ . If the current  $I$  in the primary is changing, show that the emf in the secondary is given by  $\mathcal{E}_2/\mathcal{E}_1 = N_2/N_1$ , where  $\mathcal{E}_1$  is the (back emf) of the primary.

This is a primitive transformer — a device for raising or lowering the emf of an alternating current source. By choosing the appropriate number of turns, any desired secondary emf can be achieved.

(2 points)

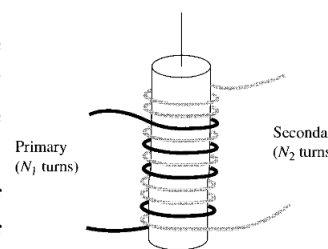

**Problem 4.** A transformer takes an input AC voltage of amplitude  $V_1$ , and delivers an output voltage of amplitude  $V_2$ , which is determined by the turns ratio,  $V_2/V_1 = N_2/N_1$  (see the previous problem). If  $N_2 > N_1$  the output voltage is greater than the input voltage. Why doesn't this violate conservation of energy? *Answer:* Power is the product of voltage and current; evidently if the voltage goes up, the current must come down.

The purpose of this problem is to see exactly how this works out, in a simplified model.

(a) In an ideal transformer the same flux passes through all turns of the primary and of the secondary. Show that in this case  $M^2 = L_1 L_2$ , where  $M$  is the mutual inductance of the coils and  $L_1$ ,  $L_2$  are their individual self-inductances.

- (b) Suppose the primary is driven with AC voltage  $V_{\text{in}} = V_1 \cos \omega t$ , and the secondary connected to a resistor with resistance  $R$ . Show that the two currents satisfy the relations

$$L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} = V_1 \cos \omega t, \quad L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = -I_2 R.$$

- (c) Using the result in (a) solve the equations for  $I_1$  and  $I_2$ . (Assume that  $I_1$  has no DC component.)
- (d) Show that the output voltage  $V_{\text{out}} = I_2 R$  divided by the input voltage  $V_{\text{in}}$  is equal to the turns ratio, *i.e.*  $V_{\text{out}}/V_{\text{in}} = N_2/N_1$ .
- (e) Calculate the input power  $P_{\text{in}} = V_{\text{in}} I_1$  and the output power  $P_{\text{out}} = V_{\text{out}} I_2$ , and show that their averages over a full cycle are equal.

(3/2 + 1 + 2 + 1 + 3/2 points)


**Problem 5.** Two coils are wrapped around each other as shown in the figure below. The current travels in the same sense around each coil. One coil has self-inductance  $L_1$ , and the other coil has self-inductance  $L_2$ . The mutual inductance of the two coils is  $M$ . Show that if the two coils are connected in parallel, the equivalent inductance of the combination is  $L = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$ .



(3 points)

**Problem 6.** In the circuit shown in the figure below, switch  $S$  is closed at time  $t = 0$  with no charge initially on the capacitor.

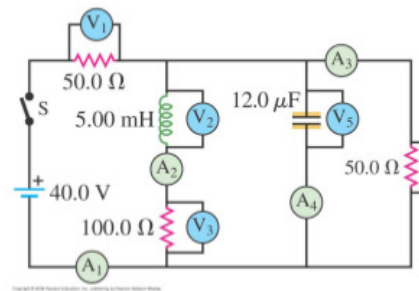- (a) Find the reading of each ammeter and each voltmeter just after  $S$  is closed.
- (b) Find the reading of each meter after a long time has elapsed.
- (c) Find the maximum charge on the capacitor.
- (d) Sketch a qualitative graph of the reading of voltmeter  $V_2$  as a function of time.



(4 × 1 point)